

Paul Kim

Lab 03



Friday section

I have spent about total 2 hours reading the "DSD lab03.pdf" lab instruction. I've tried to understand and grasp the idea fully.

Then I've first tried to write my own table, write my equations, and draw the schematic drawings. Then I've compared my answers to hint pdf. It really helped me a lot. Otherwise I might have much more hours to debug my design. Also whenever I was stuck on some problems on software or the lab itself during Thursday 2-4pm, I went to Mr. Feng's office hours 2-4pm Thursday while I was working downstairs on the computer lab. All these procedure took me about 5 hours.

Waveform simulation took me about 2 hours because my Quartus 'prime lite' on my pc was giving me node error. I've tried to figure out in my pc for awhile by remaking the project etc etc. But eventually I've gave up and decided to use the computer lab computer and rebuilt the project and I eventually got the result.

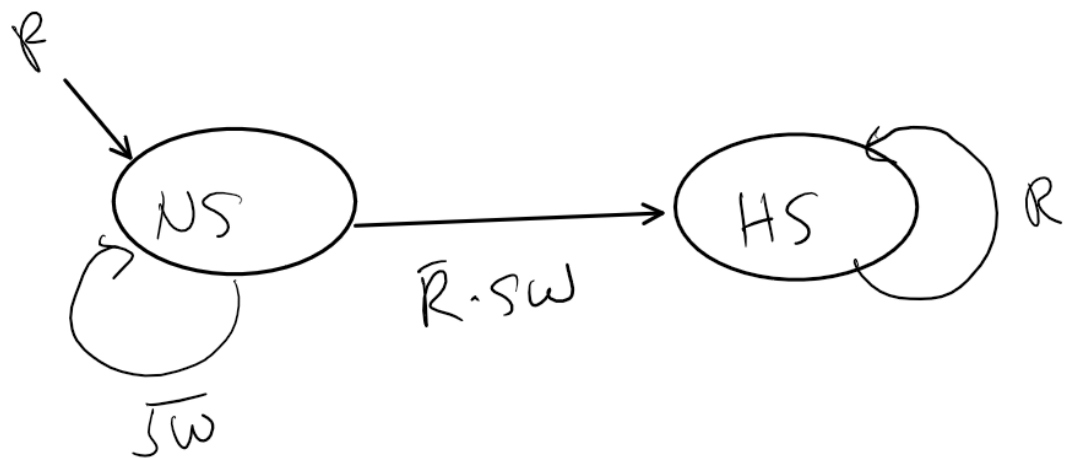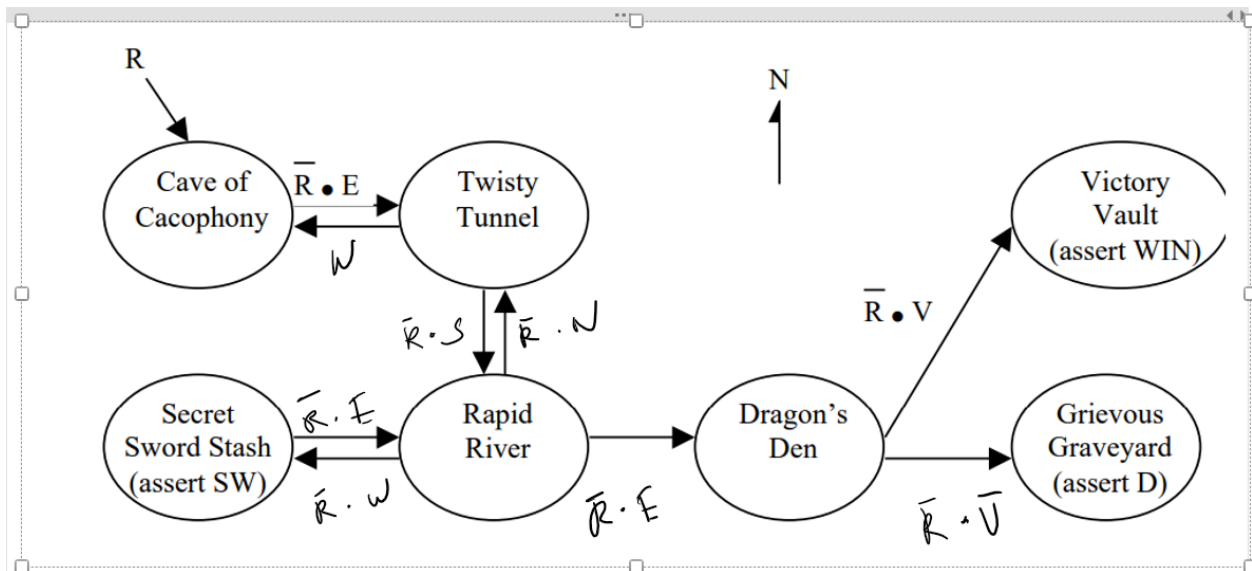So This lab took me $2+5+2=9$ hours total



Room FSM									
	state transition table								
		inputs							output
		state	N	S	W	E	R	V	state
		X	x	x	x	x	1	x	CC
		CC	x	x	x	1	0	x	TT
		TT	x	x	1	x	0	x	CC
		TT	x	1	x	x	0	x	RR
		RR	x	x	1	x	0	x	SS
		RR	x	x	x	1	0	x	DD
		RR	1	x	x	x	0	x	TT
		SS	x	x	x	1	0	x	RR
		DD	x	x	x	x	0	1	VV
		DD	x	x	x	x	0	0	GG
	output table								
		current state	sw	d	win				
		CC	0	0	0				
		TT	0	0	0				
		RR	0	0	0				
		SS	1	0	0				
		DD	0	0	0				
		VV	0	0	1				
		GG	0	1	0				

Sword FSM					
	state transition table				
		input			output
		current state	sw	R	next state
		x	x	1	NS
		NS	0	0	NS
		x	1	0	HS
		HS	x	0	HS
	output table				
		input	output		
		current state	V		
		NS	0		
		HS	1		


State encodings		
Room	CC	0000001
	TT	0000010
	RR	0000100
	SS	0001000
	DD	0010000
	GG	0100000
	VV	1000000
Sword	NS	0
	HS	1

Room FSM									
	binary state transition table								
		inputs							output
		state	N	S	W	E	R	V	state
		X	x	x	x	x	1	x	0000001
		0000001	x	x	x	1	0	x	0000010
		0000010	x	x	1	x	0	x	0000001
		0000010	x	1	x	x	0	x	0000100
		0000100	x	x	1	x	0	x	0001000
		0000100	x	x	x	1	0	x	0010000
		0000100	1	x	x	x	0	x	0000010
		0001000	x	x	x	1	0	x	0000100
		0010000	x	x	x	x	0	1	1000000
		0010000	x	x	x	x	0	0	0100000
	output table								
		current state	sw	d	win				
		0000001	0	0	0				
		0000010	0	0	0				
		0000100	0	0	0				
		0001000	1	0	0				
		0010000	0	0	0				
		0100000	0	0	1				
		1000000	0	1	0				

Sword FSM					
	binary state transition table				
		input			output
		current state	sw	R	next state
		x	x	1	0
		0	0	0	0
		x	1	0	1
		1	x	0	1
	output table				
		input	output		
		current state	V		
		0	0		
		1	1		

Sword.bdf

$$V' = (sw * \bar{R}) + (V * \bar{R})$$

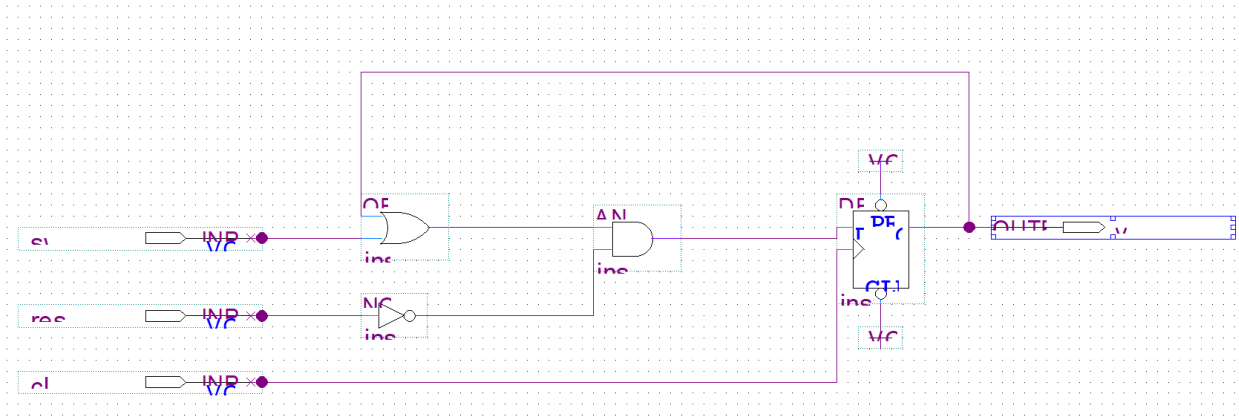

Room.bdf

Room FSM boolean equations

$$S_1' = R + S_2 W \bar{R}$$

$$S_2' = S_1 E \bar{R} + S_3 N \bar{R}$$

$$S_3' = S_2 S \bar{R} + S_4 E \bar{R}$$

$$S_4' = S_3 W \bar{R}$$

$$S_5' = S_3 E \bar{R}$$


$$S_6' = S_5 \bar{R} \bar{V}$$

$$S_7' = S_5 \bar{R} V$$


$$SW = S_4$$

$$D = S_6$$


$$Wm = S_7$$

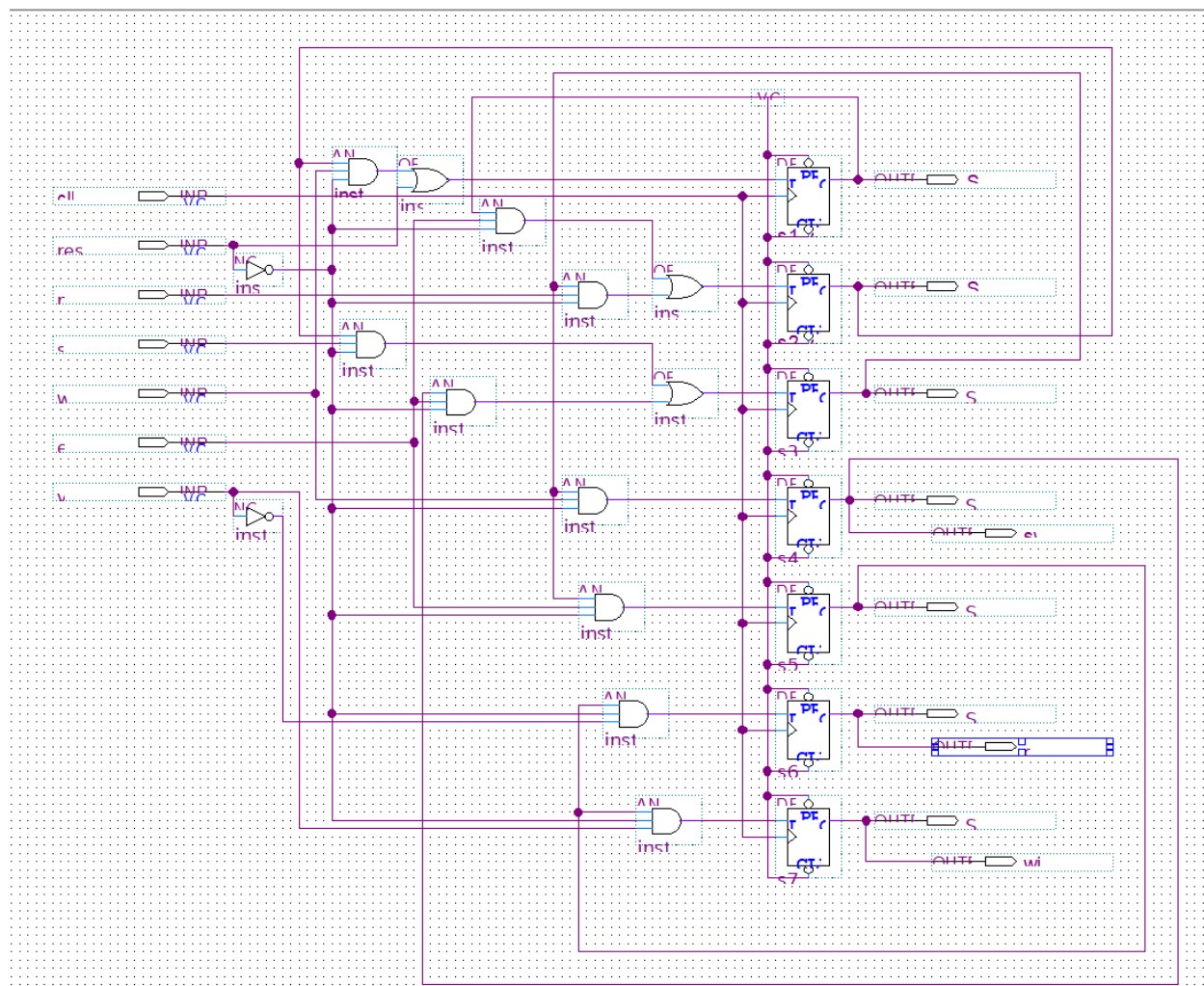

Lab03_PK.bdf

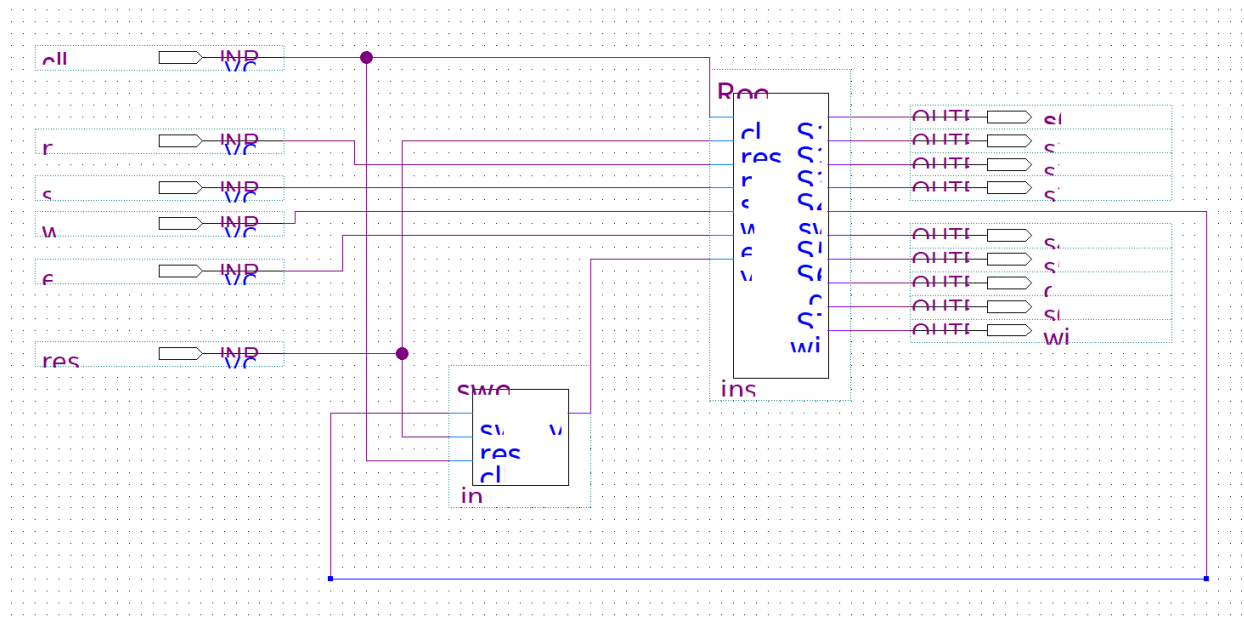

Losing game

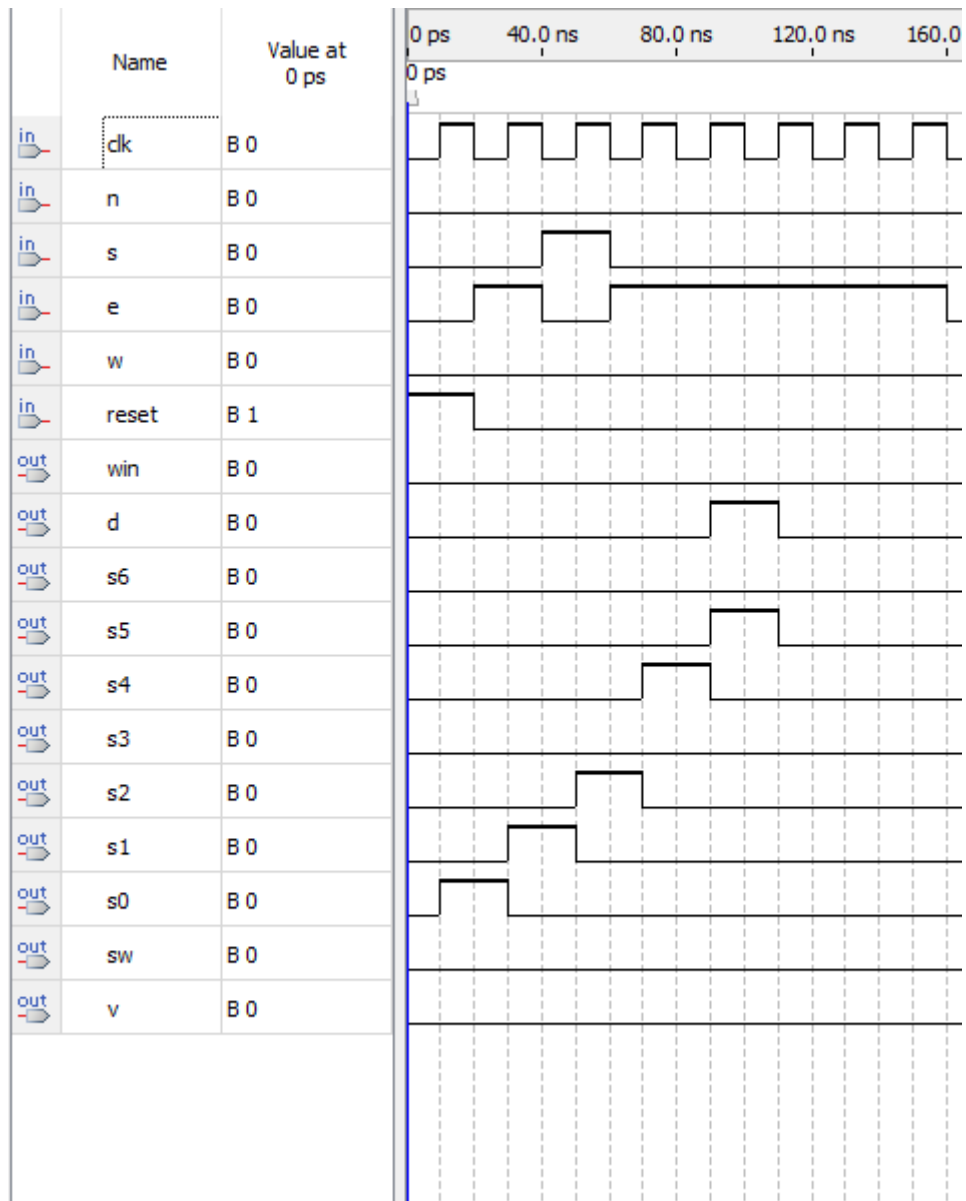

winning game

